
 


Fetch Decode Execute

Fetch Decode Execute Cycle

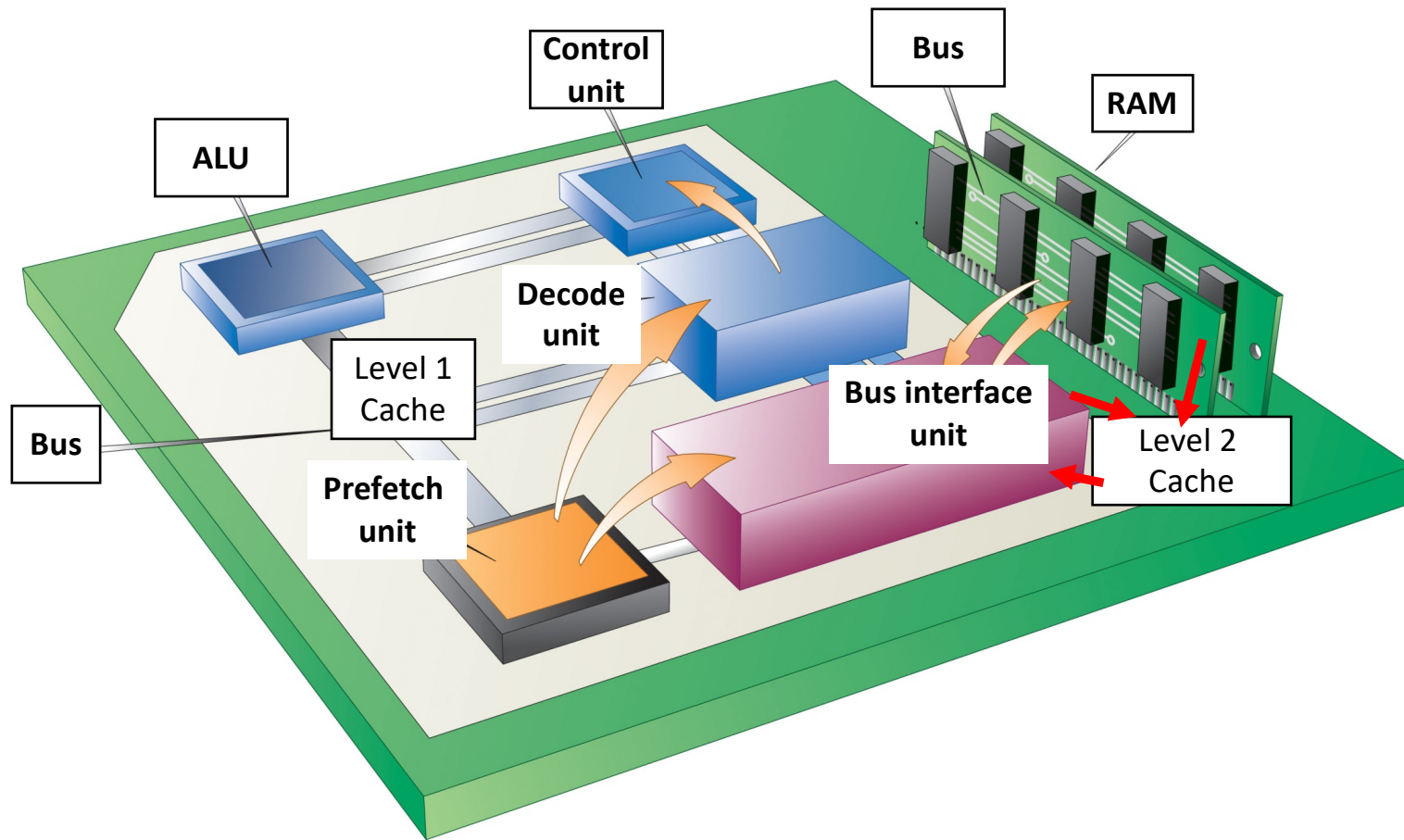



Processor Speed


Factors:

- System clock
 - # of instructions executed per second (ie. 2.5 GHz)
 - MHz is millions of cycles per second, GHz is billions
- Bus Width
 - The number of bits that can be transmitted in one clock cycle
- Word Size
 - preferred size for moving units of info (e.g. 32-bit, 64-bit)
 - Address, instruction and bus sizes are usually multiples of the word size

Architecture

- general design of CPU

A simplified representation...

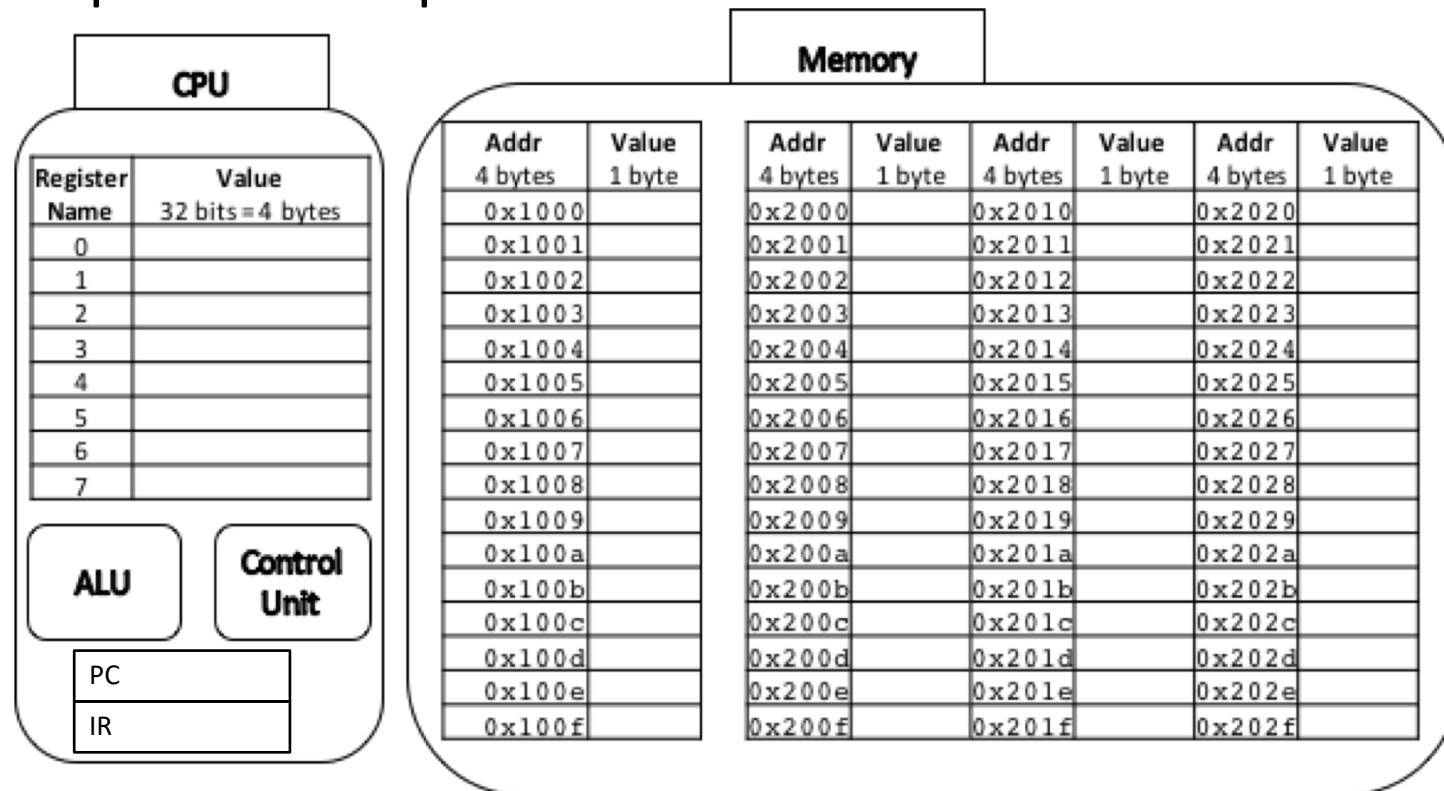


PC – Program Counter: holds the address of the next instruction

IR – Instruction Register: holds the current instruction being executed

How Registers are used in the CPU

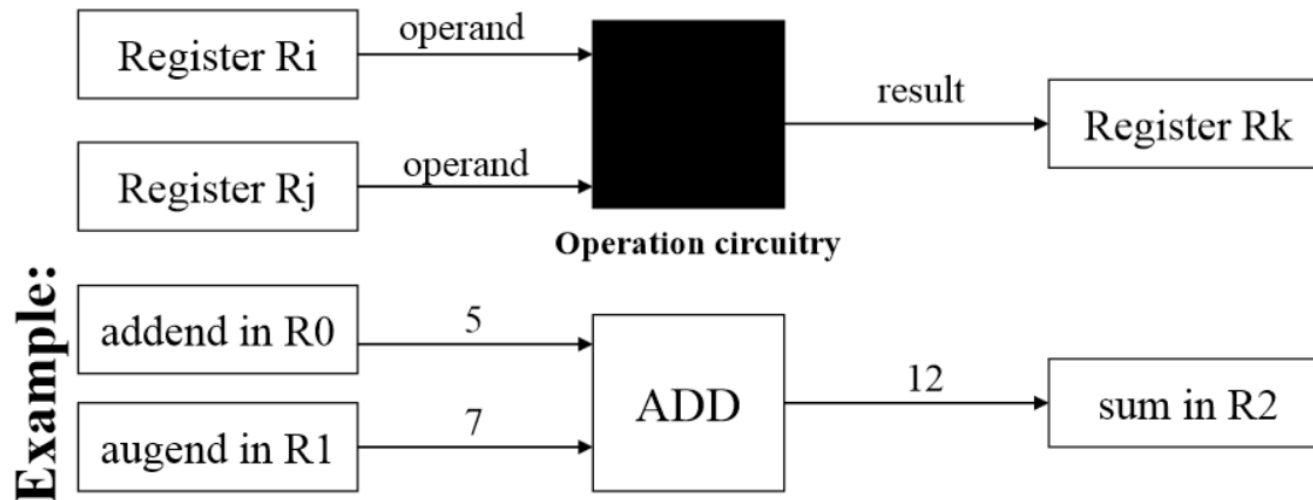- Every arithmetic or logical operation has one or more operands and one result.
- Operands are contained in registers (“source”).
- A “black box” of circuits performs the operation.
- The result goes into a register (“destination”).



Digital Logic Building Blocks

- Logic functions are implemented using basic building blocks of AND, OR, NOT, XOR
- Order of operations: BNAO

AND \wedge

NAND

OR \vee

NOR

NOT \neg

XOR \oplus


Logic

- I bring my umbrella when it is raining,
 or when the forecast is bad
 - raining, forecast bad -> umbrella
 - raining, forecast good -> umbrella
 - not raining, forecast bad -> umbrella
 - not raining, forecast good -> no umbrella

OR Truth Table (+ or V)

1 = true, 0 = false

Raining?	Forecast bad?	Umbrella (raining or forecast bad)
0	0	0
0	1	1
1	0	1
1	1	1

 

Logic

- **Or** is a logical operation
 - it means one or the other or both must be true
- **And** is also a logical operation
 - it means both must be true
- **Boolean value:** TRUE or FALSE (1 or 0)
- **Boolean expression:** An expression that is either TRUE or FALSE (1 or 0)

Logic

- I bring my umbrella if I am walking to work **and** it is raining

AND Truth Table (\bullet or \wedge)

1 = true, 0 = false


Raining?	Walking to work?	Umbrella (raining and walking)
0	0	0
0	1	0
1	0	0
1	1	1



Logic

- I bring my umbrella if I am walking to work **and** it is raining **or** the forecast is bad

 
$\text{walking} \wedge (\text{raining} \vee \text{forecast_bad})$



Truth Table

1 = true, 0 = false


Raining	Forecast bad	Walking
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

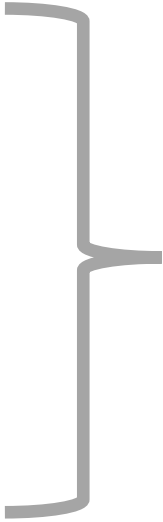

All of the possible
assignments of
binary values to
3 variables

Corresponds to the binary
encoding of 0...7 (top to bottom)

Truth Table

 


Not (x or)


— \neg

1 = true, 0 = false

A	$\neg A$
0	1
1	0

 

XOR Truth table ()

 

- XOR – only one or the other can be true

A	B	A XOR B
0	0	
0	1	
1	0	
1	1	

Test your understanding

$(X \text{ AND } Y) \text{ OR } Z$

Which assignment will make the logical expression true?

- a) $X=1, Y=0, Z=0$
- b) $X=0, Y=0, Z=1$
- c) $X=0, Y=0, Z=0$

Test your understanding

$$(X \wedge \neg Y) \vee \neg Z$$

Which assignment will make the logical expression true?

- a) $X=1, Y=0, Z=1$
- b) $X=0, Y=0, Z=1$
- c) $X=0, Y=0, Z=0$
- d) a and b
- e) a and c

Test your understanding

$$(X \wedge \neg Y) \vee \neg Z$$

Which assignment will make the logical expression true?

Lets make a truth table...

Test your understanding

$$(X \wedge \neg Y) \vee \neg Z$$

Which assignment will make the logical expression true?

- a) $X=1, Y=0, Z=1$
- b) $X=0, Y=0, Z=1$
- c) $X=0, Y=0, Z=0$
- d) a and b
- e) a and c

Compare for Equality (1 bit)

- Return 1 if two bits are equal
- Use only AND, OR and NOT

A	B	A=B?
0	0	1
0	1	0
1	0	0
1	1	1

Note the assignments that work out to true (1)

Desired Output

Compare for Equality

A	B	$A \wedge B$	$A=B?$
0	0	0	1
0	1	0	0
1	0	0	0
1	1	1	1

Compare for Equality


A	B	$A \wedge B$	$\neg A \wedge \neg B$	$A=B?$
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

Compare for Equality

A	B	$A \wedge B$	$\neg A \wedge \neg B$	$(A \wedge B) \vee (\neg A \wedge \neg B)$	A=B?
0	0	0	1	1	1
0	1	0	0	0	0
1	0	0	0	0	0
1	1	1	0	1	1

1-CE

FIGURE 4.27

 

One-bit compare-for-equality circuit

Compare for Equality (CE)

- N-bit CE circuit
- Input:
 - $a_0a_1\dots a_{n-1}$
 - $b_0b_1\dots b_{n-1}$(a_i and b_i are individual bits)
- Pair up corresponding bits:
 - a_0 with b_0
 - a_1 with b_1
 - etc.
- Run a 1-CE circuit on each pair
- Perform AND on all of the 1-CE outputs

FIGURE 4.28

